

# SIMULATION AND IMPLEMENTATION OF COMBINATIONAL LOGIC CIRCUITS

## AIM

To simulate and synthesis ENCODER, DECODER, MULTIPLEXER, DEMULTIPLEXER, MAGNITUDE COMPARATOR using Xilinx ISE

## PROCEDURE

**STEP:1** Start the Xilinx navigator, Select and Name the New project.

**STEP:2** Select the device family, device, package and speed.

**STEP:3** Select new source in the New Project and select Verilog Module as the Source type.

**STEP:4** Type the File Name and Click Next and then finish button. Type the code and save it.

**STEP:5** Select the Behavioral Simulation in the Source Window and click the check syntax.

**STEP:6** Click the simulation to simulate the program and give the inputs and verify the outputs as per the truth table.

**STEP:7** Select the Implementation in the Sources Window and select the required file in the Processes Window.

**STEP:8** Select Check Syntax from the Synthesize XST Process. Double Click in the FloorplanArea/IO/Logic-Post Synthesis process in the User Constraints process group. UCF(User constraint File) is obtained.


**STEP:9** In the Design Object List Window, enter the pin location for each pin in the Loc column Select save from the File menu.

**STEP:10** Double click on the Implement Design and double click on the Generate Programming File to create a bitstream of the design.(.v) file is converted into .bit file here.

**STEP:11** On the board, by giving required input, the LEDs starts to glow light, indicating the output.

## LOGIC DIAGRAM


\\ENCODER\\

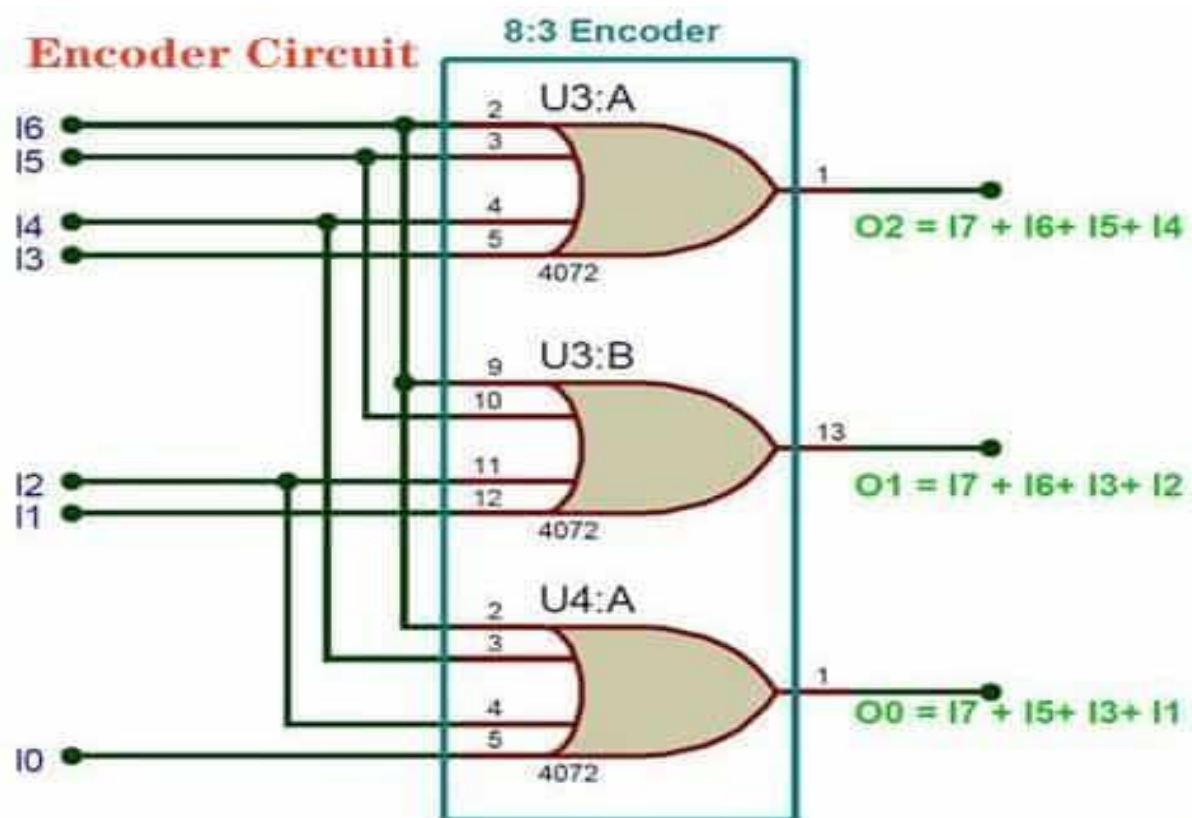

# VERILOG CODE


```
module encoder(a,y);  
  
input [7:0]a;  
  
output[2:0]y;  
  
or(y[2],a[6],a[5],a[4],a[3]);  
  
or(y[1],a[6],a[5],a[2],a[1]);  
  
or(y[0],a[6],a[4],a[2],a[0]);  
  
endmodule
```

## OUTPUT

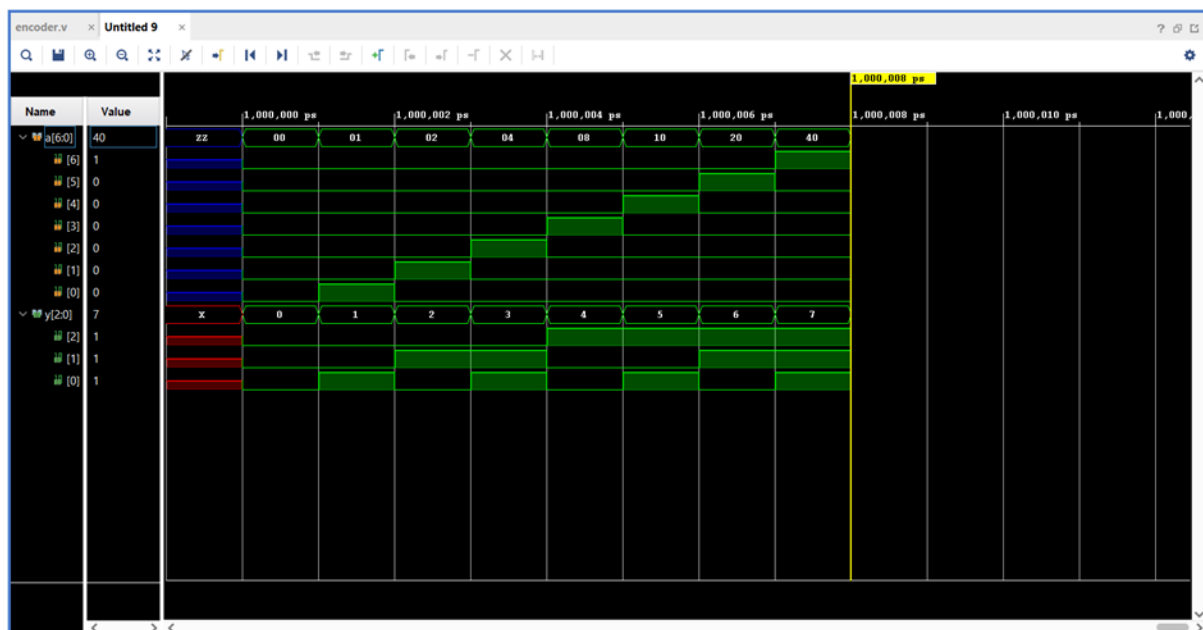

## LOGIC DIAGRAM


\\DECODER\\

 

## VERILOG CODE


```
module decoder1(a,y);  
  
input [2:0]a;  
  
output[7:0]y;  
  
and(y[0],~a[2],~a[1],~a[0]);  
  
and(y[1],~a[2],~a[1],a[0]);  
  
and(y[2],~a[2],a[1],~a[0]);  
  
and(y[3],~a[2],a[1],a[0]);  
  
and(y[4],a[2],~a[1],~a[0]);  
  
and(y[5],a[2],~a[1],a[0]);  
  
and(y[6],a[2],a[1],~a[0]);  
  
and(y[7],a[2],a[1],a[0]);  
  
endmodule
```

# OUTPUT

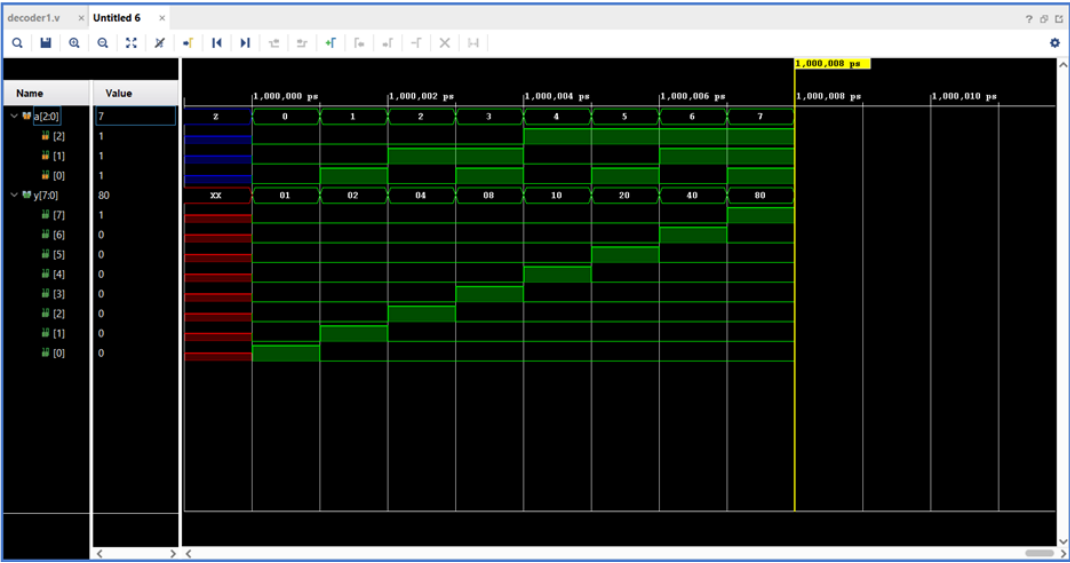

# LOGIC DIAGRAM


\\ MULTIPLEXER \\

 

## VERILOG CODE


```
module mux(s,c,a);  
input [2:0]s;  
input [7:0]a;  
wire [7:0]w;  
output c;  
and(w[0],a[0],~s[2],~s[1],~s[0]);  
and(w[1],a[1],~s[2],~s[1],s[0]);  
and(w[2],a[2],~s[2],s[1],~s[0]);  
and(w[3],a[3],~s[2],s[1],s[0]);  
and(w[4],a[4],s[2],~s[1],~s[0]);  
and(w[5],a[5],s[2],~s[1],s[0]);  
and(w[6],a[6],s[2],s[1],~s[0]);  
and(w[7],a[7],s[2],s[1],s[0]);  
or (c,w[0],w[1],w[2],w[3],w[4],w[5],w[6],w[7]);  
endmodule
```

# OUTPUT

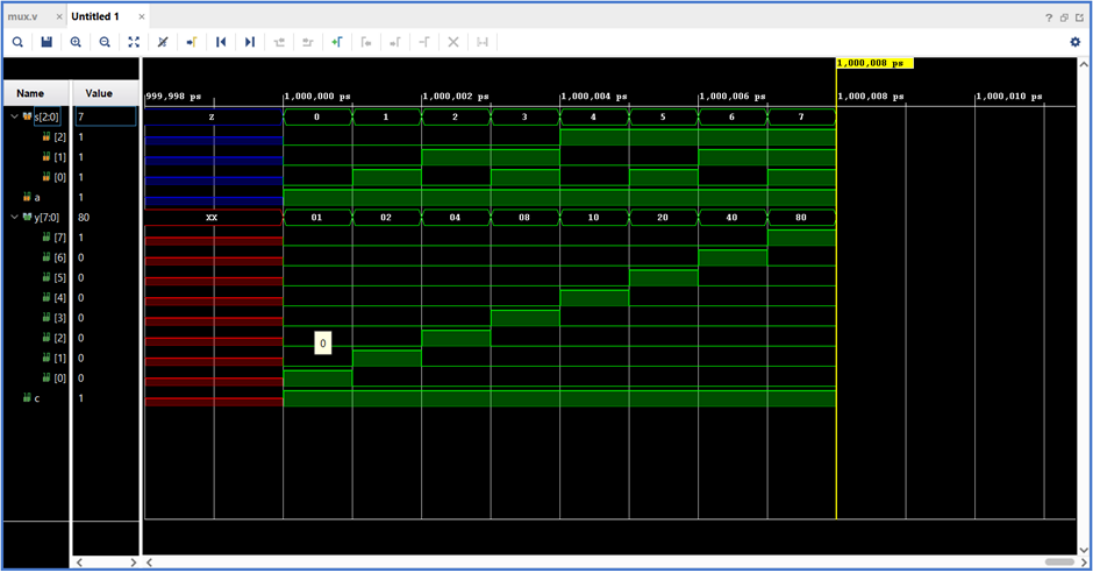

# LOGIC DIAGRAM

## //DEMULTIPLEXER//

 




## VERILOG CODE

```
module demux_8(s,a,y);  
input [2:0]s;  
input a;  
output [7:0]y;  
and(y[0],a,~s[2],~s[1],~s[0]);  
and(y[1],a,~s[2],~s[1],s[0]);  
and(y[2],a,~s[2],s[1],~s[0]);  
and(y[3],a,~s[2],s[1],s[0]);  
and(y[4],a,s[2],~s[1],~s[0]);  
and(y[5],a,s[2],~s[1],s[0]);  
and(y[6],a,s[2],s[1],~s[0]);  
and(y[7],a,s[2],s[1],s[0]);  
endmodule
```

# OUTPUT

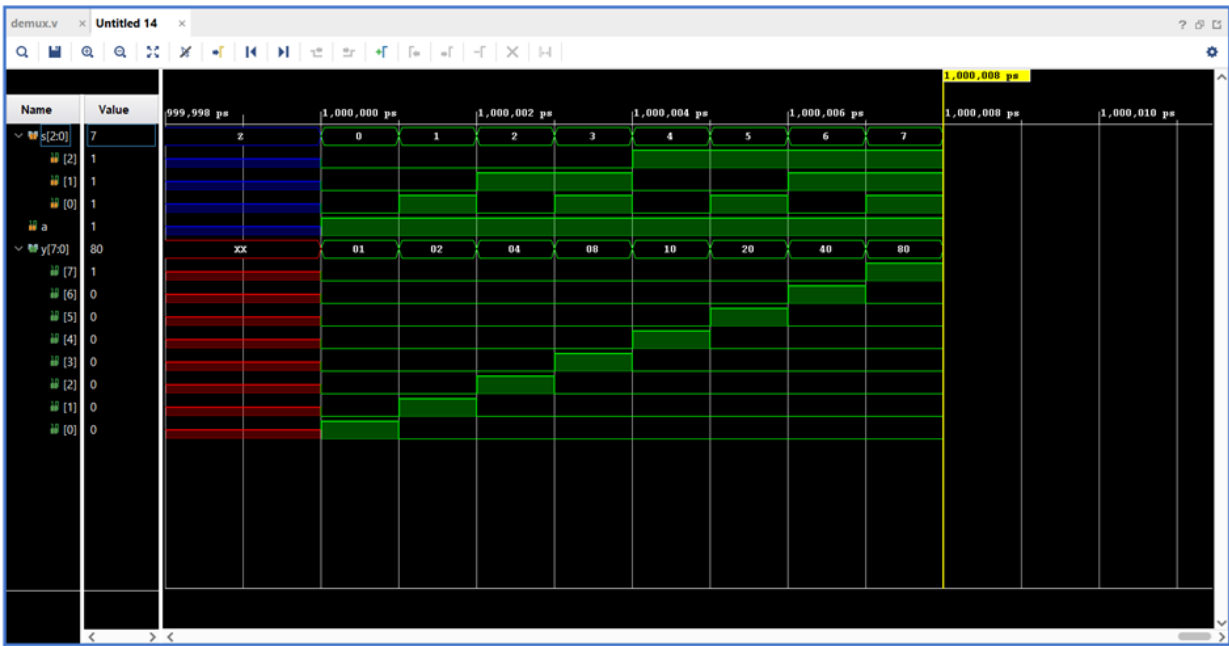

# LOGIC DIAGRAM

\\MAGNITUDE COMPARATOR\\




## VERILOG CODE

```
module comparator(a,b,eq,lt,gt);  
input [3:0] a,b;  
output reg eq,lt,gt;  
always @(a,b)  
begin  
if (a==b)  
begin  
eq = 1'b1; lt = 1'b0; gt = 1'b0;  
end  
else if (a>b)  
begin  
eq = 1'b0; lt = 1'b0; gt = 1'b1;  
end  
else  
begin  
eq = 1'b0; lt = 1'b1; gt = 1'b0;  
end  
end
```

end

endmodule

## OUTPUT

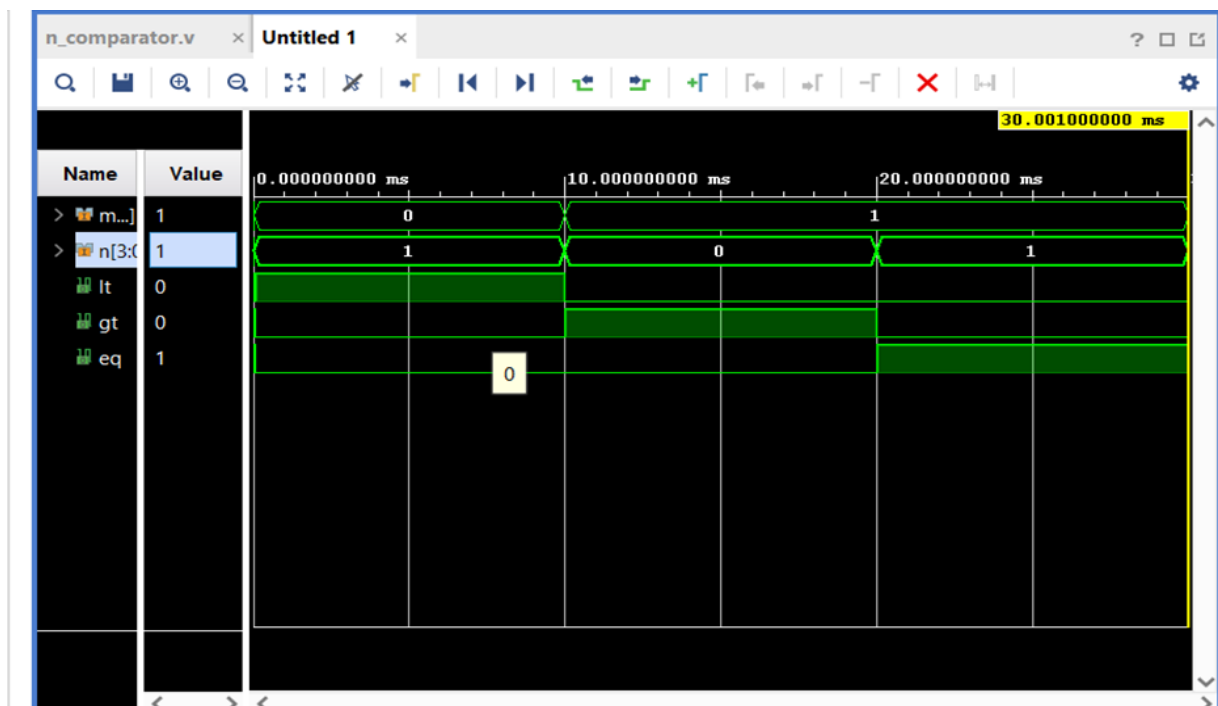

## RESULT

Thus The Simulate And Synthesis Encoder, Decoder, Multiplexer, Demultiplexer, Magnitude Comparator Using Xilinx Ise Are Verified Successfully